

Project 6: Controlling LEDs using IR Remote and Arduino UNO on TinkerCAD

The components used in this project are:

1. Arduino Uno

- Main microcontroller board used to run the code and control the LEDs.

2. Breadboard

- Used to connect and organize the circuit without soldering.

3. IR Remote

- Used to send signals to the IR sensor.

4. IR Receiver Sensor (TSOP or similar)

- Receives the signals from the IR remote.

5. LEDs (3 Total):

- **1x Blue LED**
- **1x Orange LED**
- **1x Green LED**
- Used as output indicators based on remote input.

6. Resistors (3x 220 ohms)

- Connected in series with each LED to limit current and prevent damage.

7. Jumper Wires

- Used for connections between the Arduino, breadboard, and componen

Description :

1. Connect the LEDs:

- **Anodes** (longer leg) of the three LEDs are connected to:
 - Blue LED → **Pin 2**

- Orange LED → **Pin 3**
- Green LED → **Pin 4**
(All on the Arduino UNO board)

2. Resistors and Grounding:

- **Cathodes** (shorter leg) of each LED are connected to **220-ohm resistors**, and the other ends of the resistors go to the **GND rail** of the breadboard.

3. IR Sensor Wiring:

- **Middle terminal (GND)** of the IR sensor → **GND** of the Arduino.
- **Third terminal (VCC)** of the IR sensor → **+5V** of the Arduino.
- **First terminal (OUT)** of the IR sensor → **Pin 12** of the Arduino.

6. Common Ground:

- **GND pin** of the Arduino board is also connected to the **GND rail** of the breadboard to ensure a common ground reference.